

18002141



18002141



Reg. No.....

Name.....

**M.Sc. DEGREE (C.S.S.) EXAMINATION, DECEMBER 2018**

**First Semester**

Faculty of Science

Branch II : Physics (A)–Pure Physics

PHI C04—ELECTRONICS

(2012 Admission onwards)

Time : Three Hours

Maximum Weight : 30

**Part A**

*Answer any **six** questions.  
Each question carries 1 weight*

1. What do you meant by Differential amplifier ?
2. List the applications of FET.
3. Define CMRR.
4. What are the difference between input offset voltage and input offset current ?
5. Write short notes on AC amplifier and DC amplifier.
6. What do you mean by slew rate ?
7. Explain about VCO.
8. What are the difference between Schmitt trigger and zero crossing detector ?
9. Draw the pin out diagram of IC565-PLL.
10. What is AGC ?

(6 × 1= 6)

**Part B**

*Answer any **four** questions.  
Each question carries 2 weight.*

11. Draw the circuit diagram of inverting amplifier. Derive the expression far output voltage.  
Design an inverting amplifier for a pass band gain of 5dB.
12. Design a peaking amplifier circuits to provide a gain of 5 at a peak frequency of 12 KHz.
13. What are the different classifications of filter ? With the help of circuit diagram and frequency response explain the working of Notch filter.

**Turn over**





18002141

14. With the help of suitable diagrams explain the working of Sample and Hold Circuit.
15. Design an 8 V output voltage with the help of 78XX.
16. Write notes on the working of super heterodyne receiver.

(4 × 2 = 8)

### Part C

*Answer all questions.  
Each question carries 4 weight.*

17. (a) With the help of suitable block diagram, explain the working and characteristics of OP amp.

*Or*

- (b) List the characteristics of ideal op amp. Derive the expressions for (i) Bandwidth with feedback ; (ii) Closed loop voltage gain ; and (iii) input and output resistance.

18. (a) Draw the circuit diagram of instrumentation amplifier using transducer bridge and explain its working.

*Or*

- (b) With the help of suitable circuit diagram and frequency response explain the working of op-amp differentiator. Derive the various expressions for op-amp differentiator.

19. (a) What do you mean by Oscillator ? Draw the circuit diagram of RC phase shift oscillator and explain its working with the help of output waveforms.

*Or*

- (b) Explain the working of any two types of D/A converter

20. (a) Draw the internal architecture of IC555 and draw the circuit diagram of any one application and design the circuit.

*Or*

- (b) With the help of suitable diagrams explain about the working of FM receiver.

(4 × 4 = 16)

